

Real, Apparent and Reactive Power

Malabika Basu

Real Power (P)

- Real Power (P) measured in Watts is required to do useful work
 - Boil kettles, turn motors, power light bulbs.
 - Single phase $P = |V|.|I|.cos(\phi)$
 - Three phase $P = 3.|V_{LN}|.|I|.cos(\phi)$
or $P = \sqrt{3}.|V_{LL}|.|I|.cos(\phi)$
- Note: Real power is actually the average of instantaneous power.

Apparent Power (S)

- The apparent power (S) measured in VA is just the product of (rms) Volts and (rms) Amps
 - The apparent power (S) is a useful figure for determining the size of electrical equipment.
 - Single phase $S = |V| \cdot |I|$
 - Three phase $S = 3 \cdot |V_{LN}| \cdot |I|$
or $S = \sqrt{3} \cdot |V_{LL}| \cdot |I|$

Reactive Power (Q)


- You should know by now that inductors and capacitors don't dissipate any power ($\cos(\phi) = 0$) but they still draw current.
- Reactive power (Q) measured in vars is an indication of how much current is being drawn by inductors and capacitors.
 - Single phase $Q = |V|.|I|. \sin(\phi)$
 - Three phase $Q = 3. |V_{LN}|. |I|. \sin(\phi)$
or $Q = \sqrt{3}. |V_{LL}|. |I|. \sin(\phi)$
- By convention
 - Inductors draw positive vars (Q positive)
 - Capacitors draw negative vars (Q negative)

Examples

- Resistor: $\phi = 0^\circ$
 - $P = |V| \cdot |I|$
 - $S = |V| \cdot |I|$
 - $Q = 0$
- Inductor: $\phi = 90^\circ$ Lagging
 - $P = 0$
 - $S = |V| \cdot |I|$
 - $Q = +|V| \cdot |I|$
- Capacitor: $\phi = 90^\circ$ Leading
 - $P = 0$
 - $S = |V| \cdot |I|$
 - $Q = -|V| \cdot |I|$

Relationships

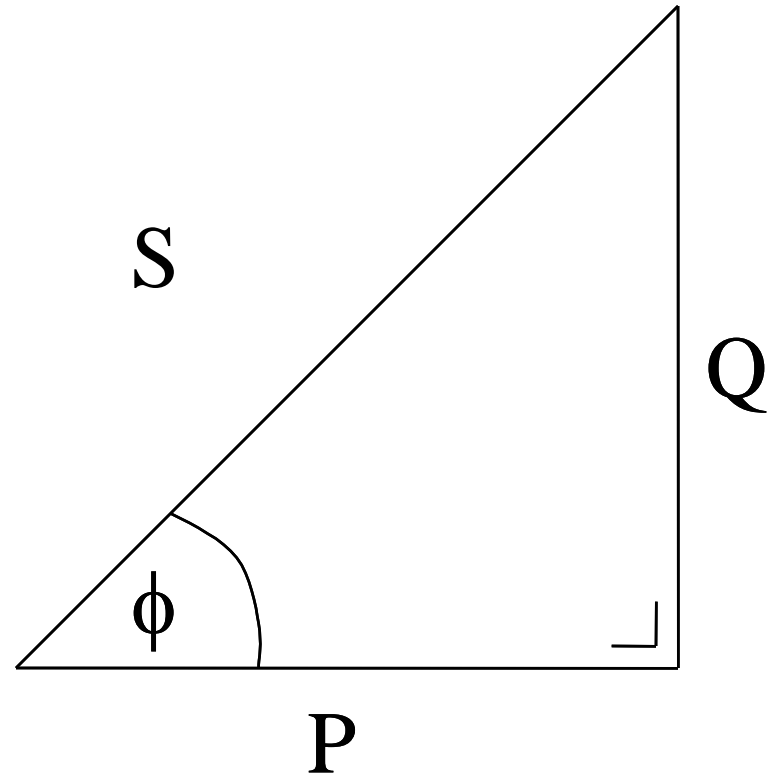
- $P = S \cdot \cos(\phi)$
 $Q = S \cdot \sin(\phi)$
 $S^2 = P^2 + Q^2$
- See the power triangle:
- **NB: $\cos(\phi)$ is usually called the Power Factor or PF for short.**



Power factor correction

- High Q (lots of inductors or capacitors) is a bad thing.
 - High $Q \Rightarrow$ low power factor
 - For a given level of useful work a high Q will require higher S and higher current \Rightarrow higher losses in transmission.
- Utilities (ESB) penalise industrial users if their power factor falls below 0.95
 - Unfortunately most industrial loads (e.g. motors and transformers) have high inductance \Rightarrow low power factor
 - Luckily you can add capacitors (negative Q) to cancel out the positive Q of inductors.

Power Factor Correction

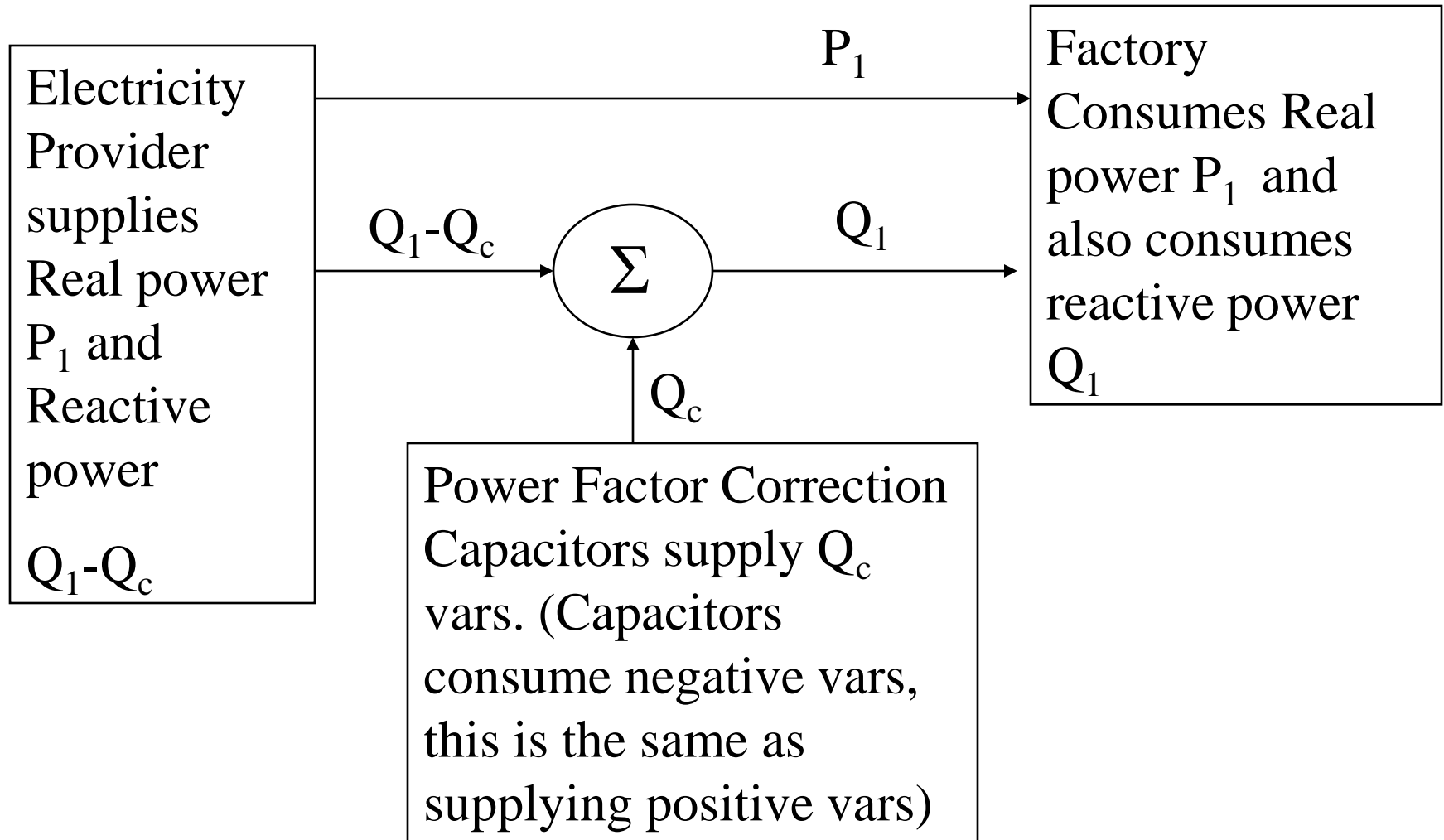

Question

- A factory draws 1MVA at a power factor of 0.8 lagging from a 10kV 3 phase supply.
- What is the current drawn from the supply?
- How many vars of power factor correction capacitance are required to bring the power factor up to 0.95?
- What will the new current be after the capacitors are fitted?