



SIMULATION FOR MACHINES

LAB 1

DT021A/3 Electrical Machine



SEPTEMBER 30, 2020

TALHA TALLAT
D18124645

Model 1:

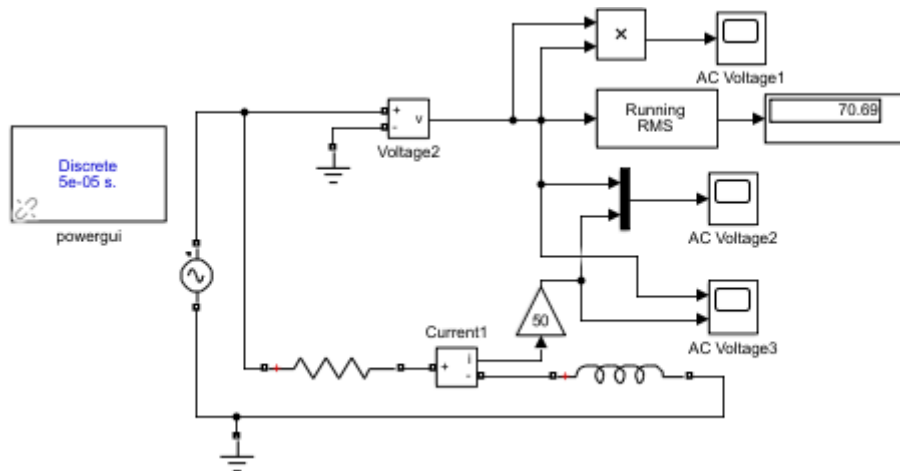


Figure 1 - Schematic diagram of the simple single-phase circuit

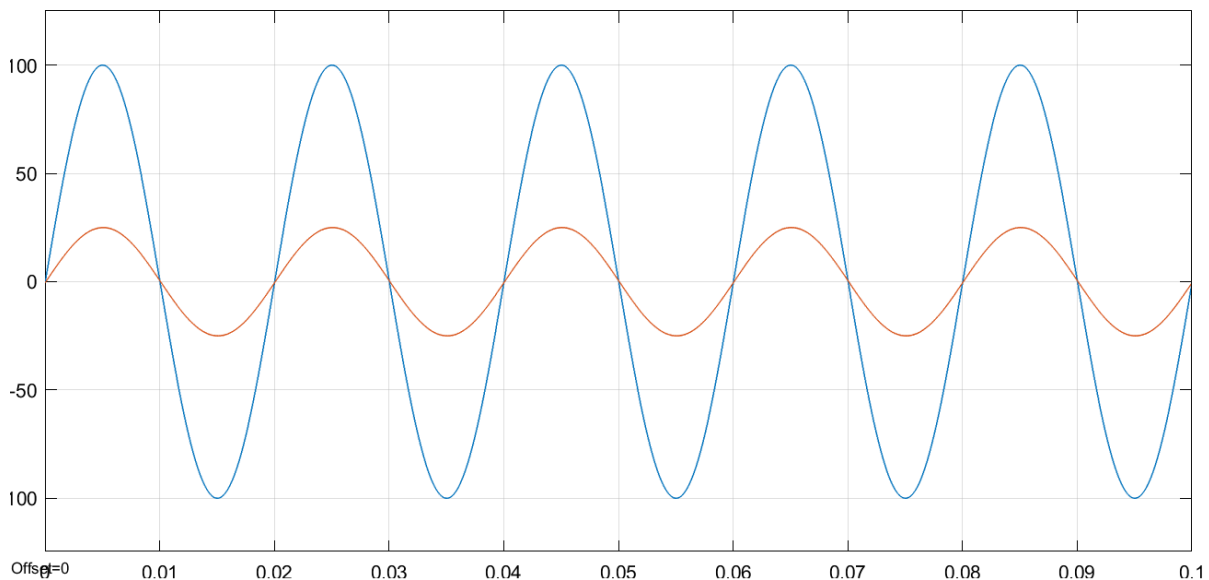


Figure 2 - Output voltage and current peak amplitude of single-phase circuit

The sinusoidal signal with a voltage amplitude of 100vpp is applied to the circuit with the frequency of 50Hz. The output current is in phase with output voltage.

The V_{rms} value of the AC signal is given by $\frac{1}{\sqrt{2}}$. The Block diagram shows the V_{rms} value of 70.69Vrms which satisfies the calculated value of 70.7Vrms.

$$V_{rms} = 100 * \frac{1}{\sqrt{2}} = 70.7$$

Simulation stop time is set to 0.1s to see the 5 number of cycles at the output. The following equation is used to have 5 cycles and figure 2 shows the 5 cycles.

$$p = \frac{1}{f} = \frac{1}{50Hz} = 0.02s$$

$$Cycles = \frac{0.1s}{0.02s} = 5$$

To measure the power of the

Model 2:

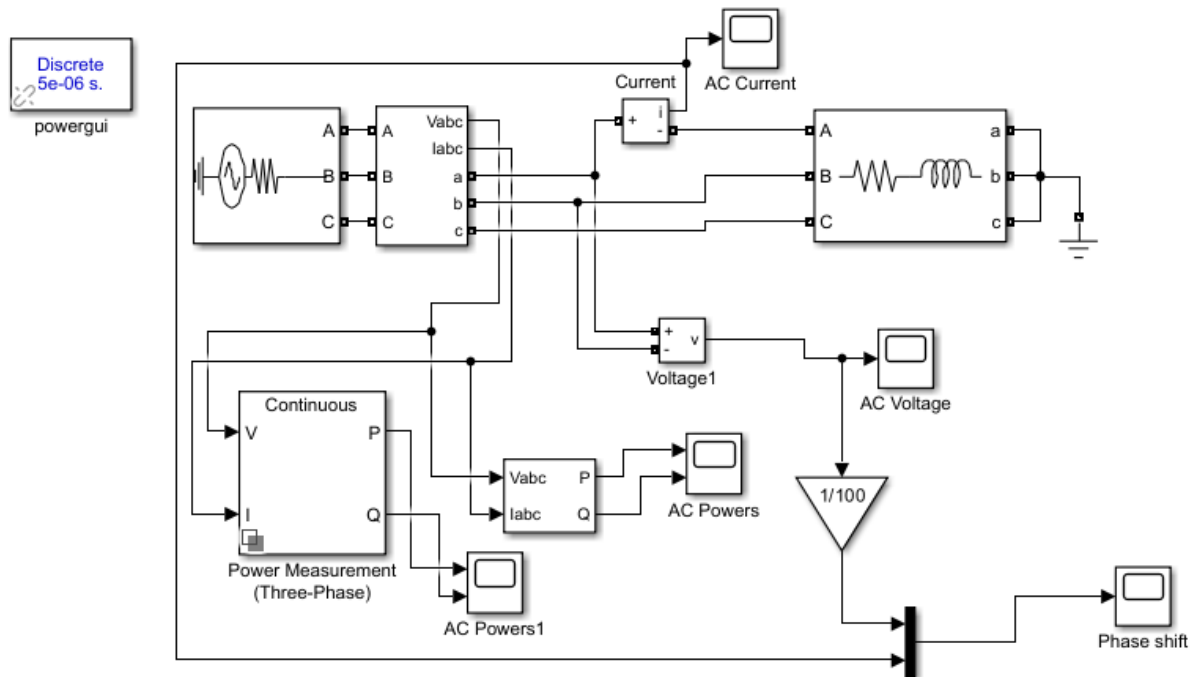


Figure 3 - Schematic diagram of the 3-phase circuit

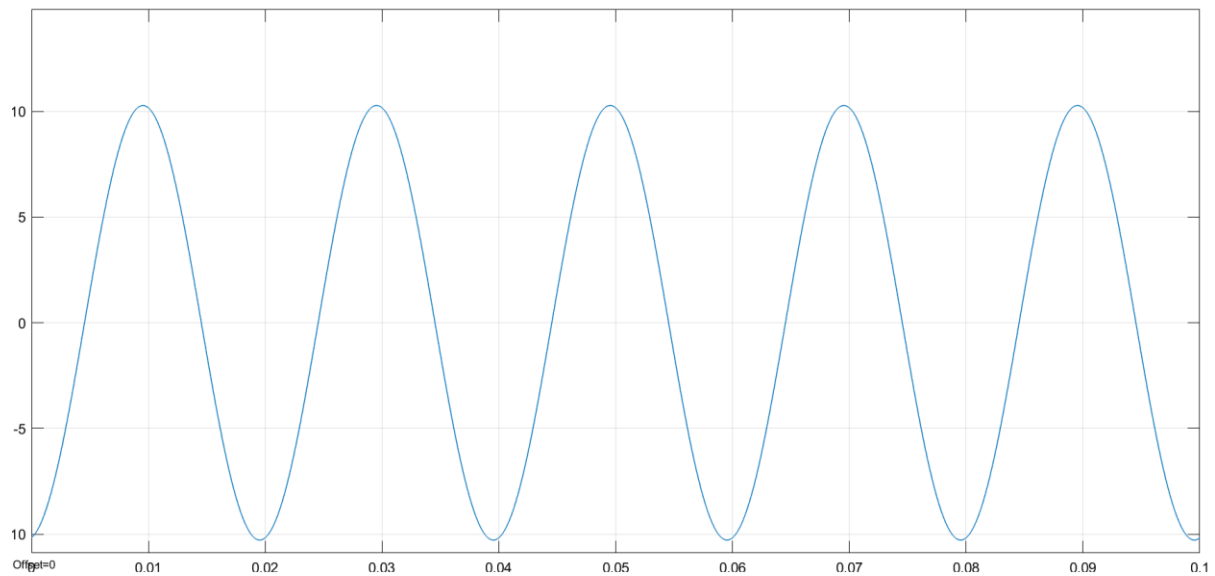


Figure 4 - Current Measurement for the 3-phase circuit

The AC current in phase 1 has amplitude from -10 to 10A and oscillates every 20ms.

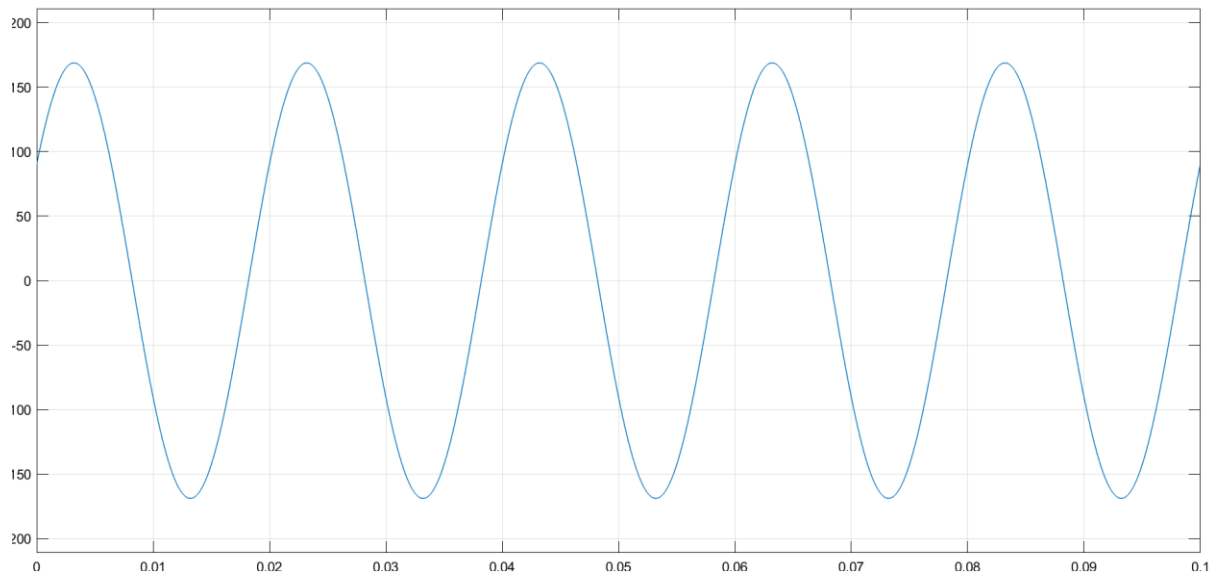
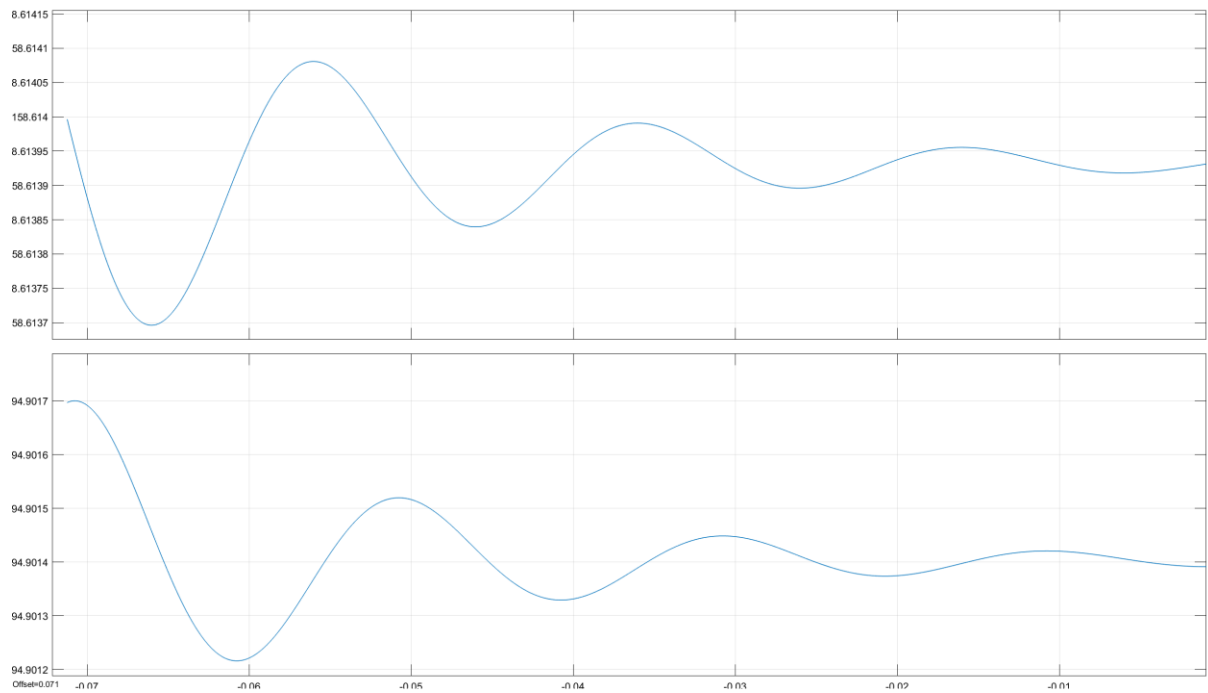


Figure 5 - Voltage Measurement

Peak amplitude is 168Vpp.

$$\begin{aligned}
 \Rightarrow V_{ab} &= V - V \{ \cos(-120^\circ) + j \sin(-120^\circ) \} \\
 &= V - V \left\{ -0.5 - j \frac{\sqrt{3}}{2} \right\} \\
 &= V \left[1 - \left\{ -0.5 - j \frac{\sqrt{3}}{2} \right\} \right] \\
 &= V \left[1 + 0.5 + j \frac{\sqrt{3}}{2} \right] \\
 &= V \left[\frac{3}{2} + j \frac{\sqrt{3}}{2} \right] = \sqrt{3} V \left[\frac{\sqrt{3}}{2} + j \frac{1}{2} \right] = \sqrt{3} V \angle 30^\circ \\
 \Rightarrow V_{ab} &= \sqrt{3} V \angle 30^\circ
 \end{aligned}$$

Figure 6 - AC power – V_a & I_a

$$P = 3 V_p * I_p * \cos\theta$$

$$P = 3 (168) * (10) * \cos$$

$$P = 5.04\text{kW}$$

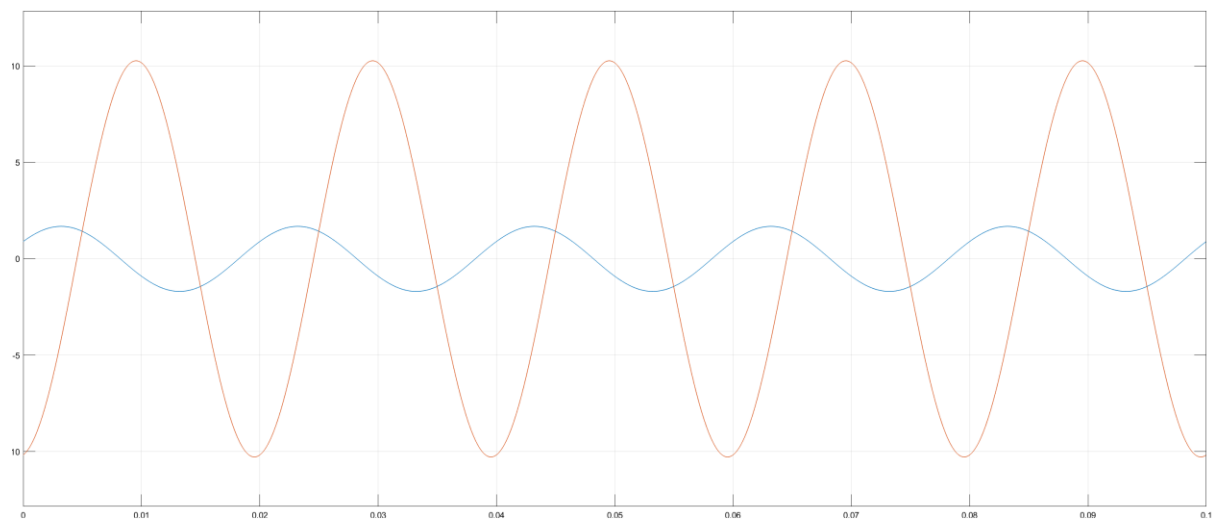


Figure 7 - Phase shift between current and voltage

The output voltage (168Vpp) has dropped due to the very small gain (1/100) and the voltage waveform is shifted by 90 degrees.

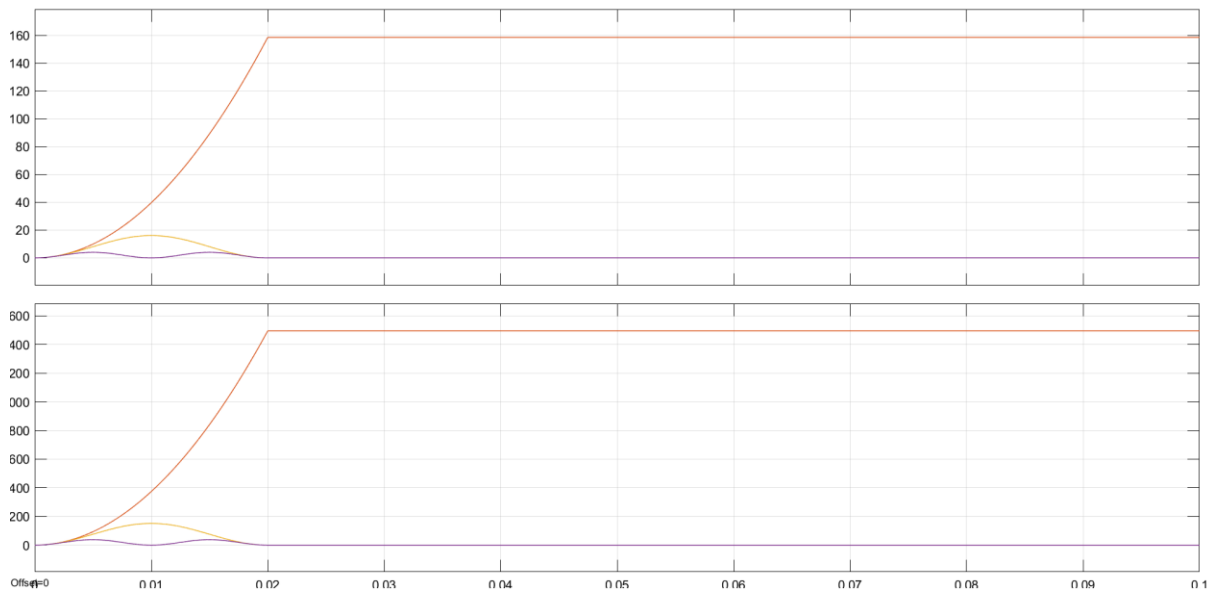


Figure 8 - Power Measurements when using the power block

$$V_{rms} = 125 * \frac{1}{\sqrt{2}} = 88.38$$

For the Δ -load :

$$I_A = \sqrt{3} I_{AB} \angle -30^\circ = \frac{\sqrt{3} \cdot E_{AB} \angle -30^\circ}{Z_{\Delta}}.$$

For the Y -load :

$$I_A = \frac{E_{AN}}{Z_y} = \frac{E_{AB} \angle -30^\circ}{\sqrt{3} Z_y}$$

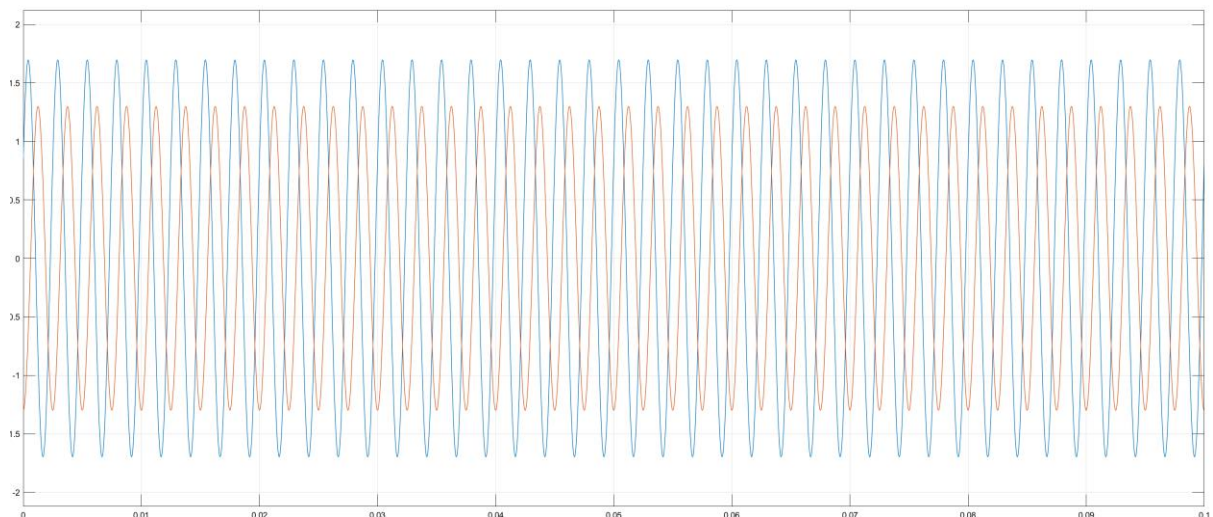


Figure 9 – increasing the frequency by 400Hz

The amplitude and phase stay the same only the cycles increase when increasing the frequency.

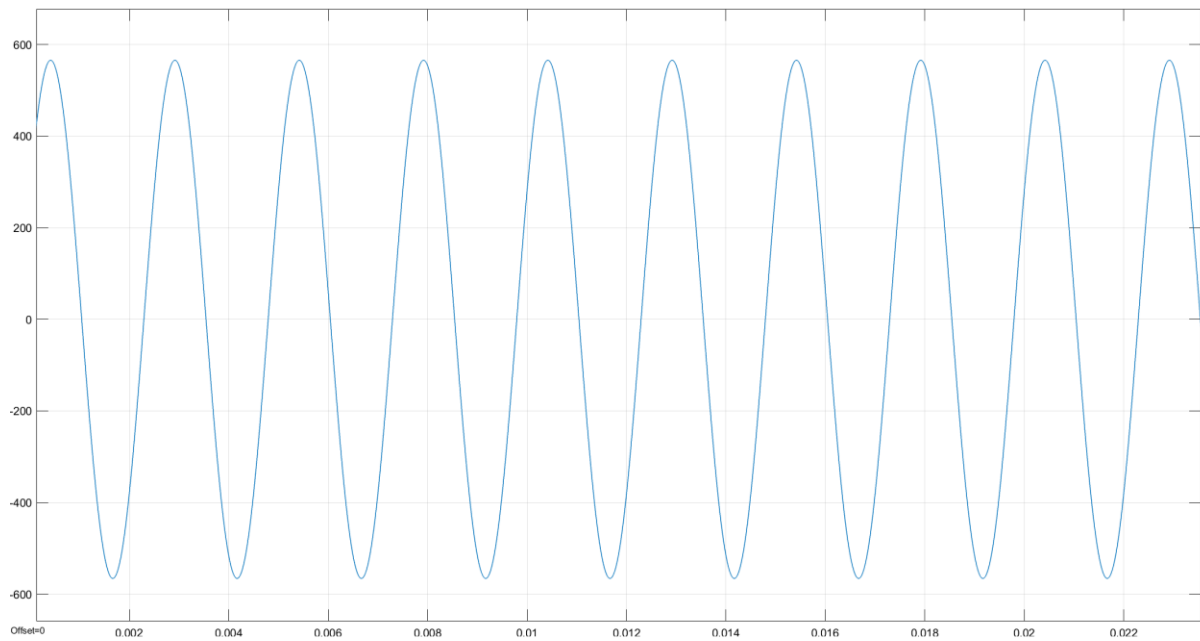


Figure 10 - The output voltage increases to 570v when the input volts increases to 400v

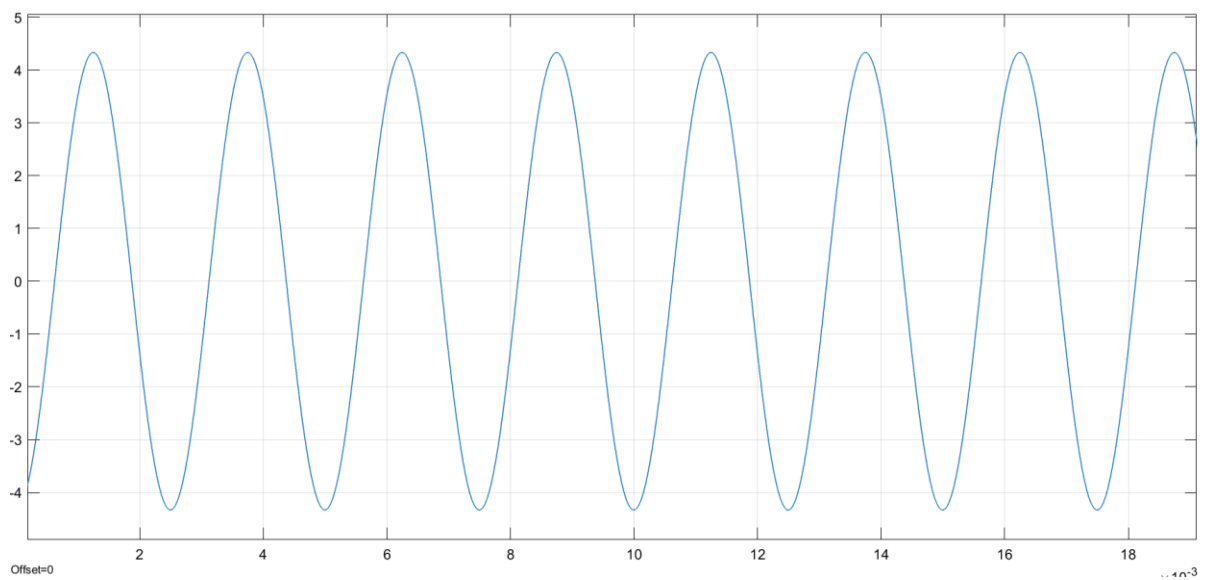


Figure 11 - Current decreases when applying 400v sinusoidal input

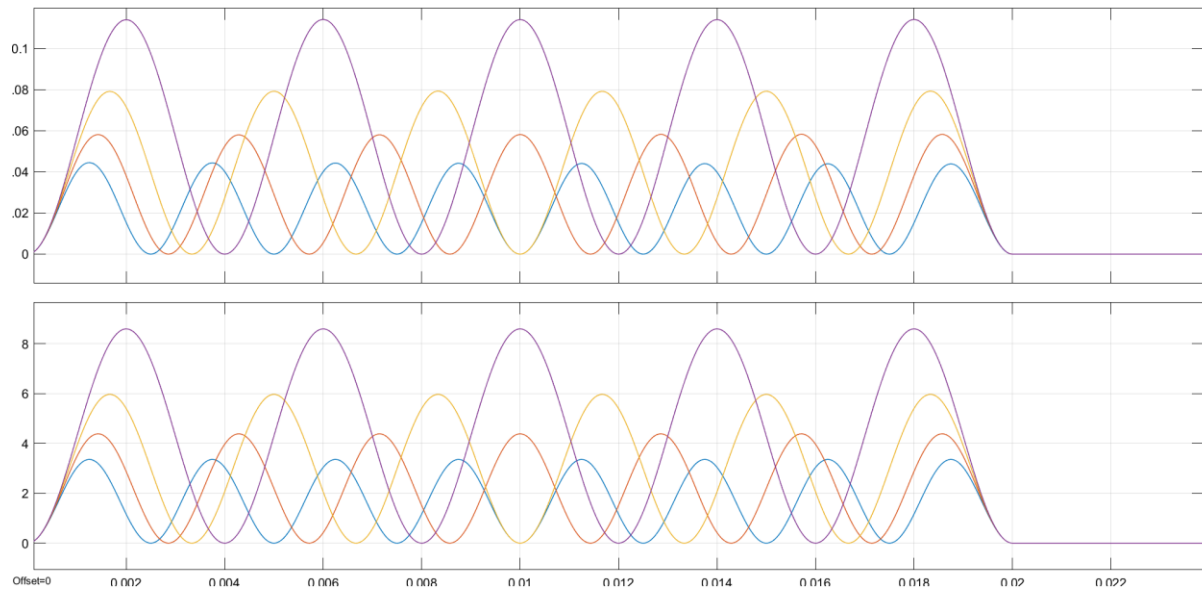


Figure 12 - 3 phase power measurements