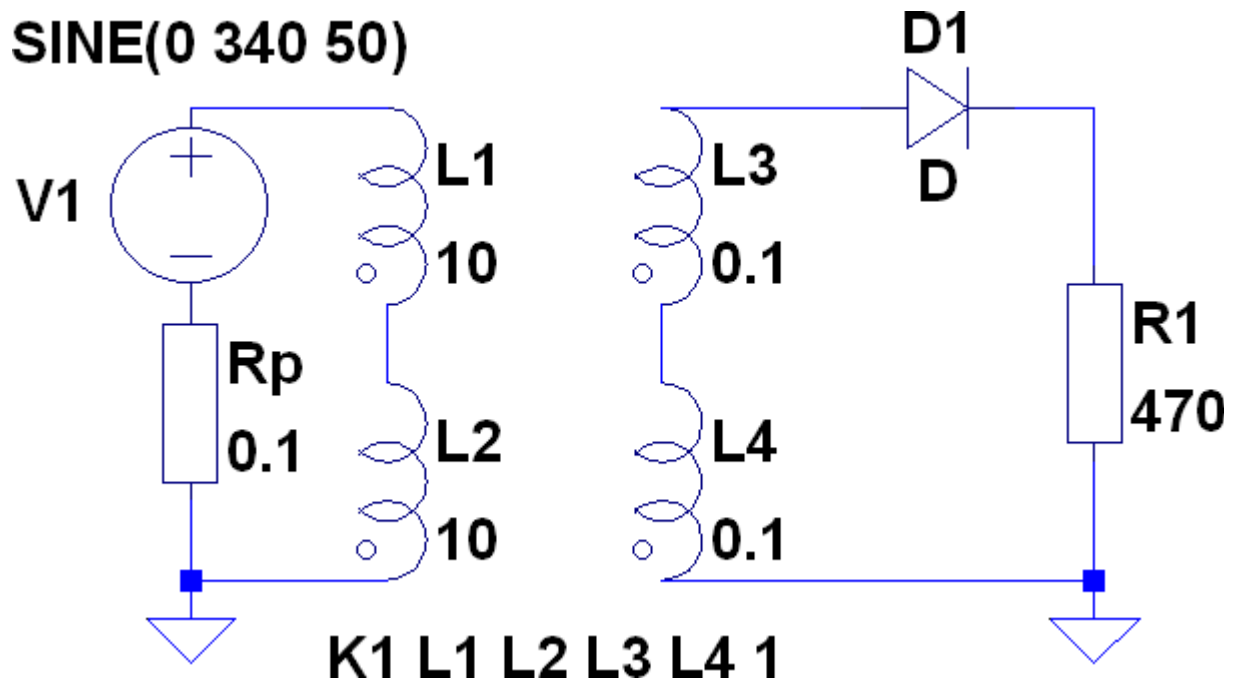


Rectifier circuits.

Half wave rectifier:

These are rarely used in practice. They draw unipolar current from the transformer which can lead to magnetization and hence saturation of the core.



Ltspice notes.


The resistor R_p in the diagram below is included to eliminate a voltage/inductor loop which SPICE is unable to simulate.

*Transformers are modelled as coupled inductors. The SPICE directive **K1 L1 L2 ...** above defines the coupling between the inductors. A coupling factor of '1' implies perfect coupling so there is no leakage inductance.*

The square root of the inductance ratio = turns ratio


Push-Pull (Centre-tapped) Full wave rectifier

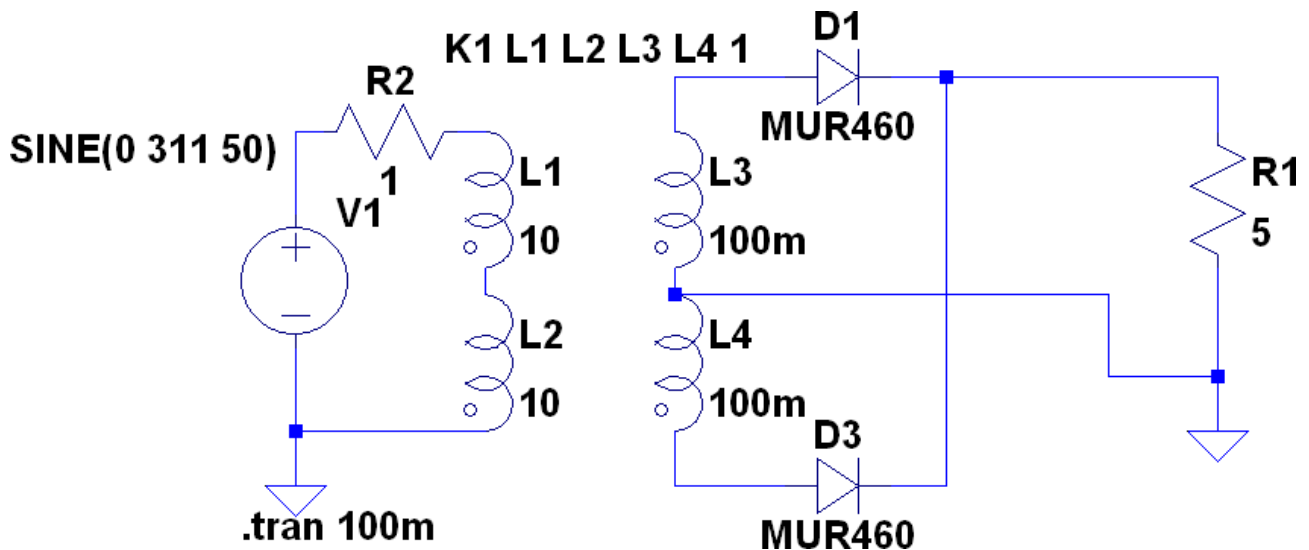This rectifier requires a transformer with a pair of secondary windings or a single winding with a centre tap. It uses only 2 diodes. Each diode conducts during alternative half cycles.



Full wave bridge rectifier

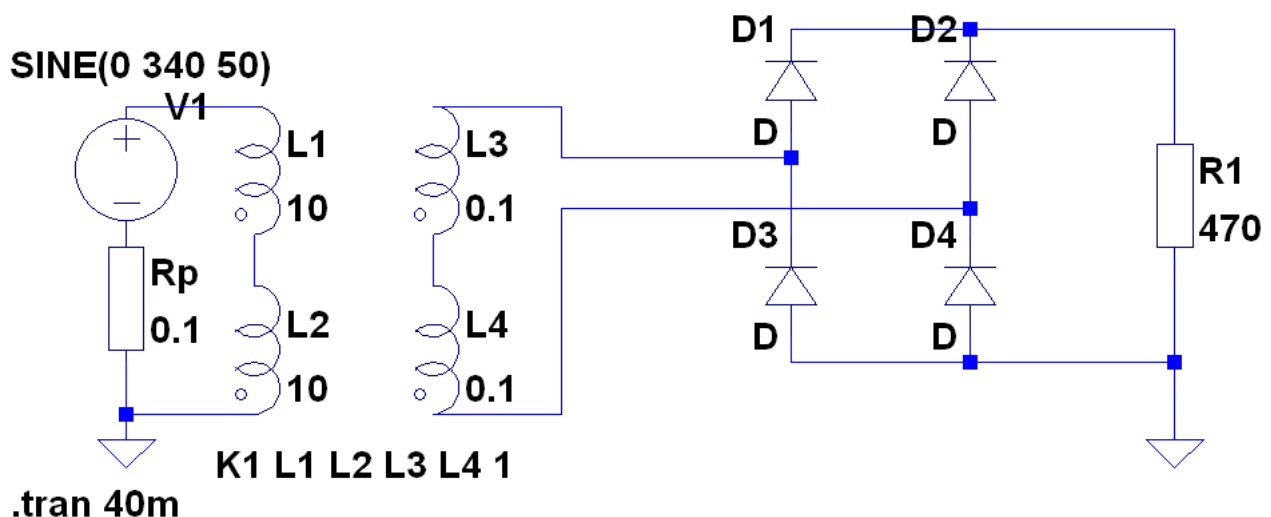This rectifier uses 4 diodes as shown below. Often the diodes are contained in a single 4 terminal package (a bridge rectifier). Diagonally opposite diodes conduct in alternative half cycles.



Full wave bipolar bridge rectifier.

This circuit is similar to the bridge rectifier but requires a centre tap on the secondary winding. It is used to create a bipolar DC supply (e.g. +15,0,-15 supply).

