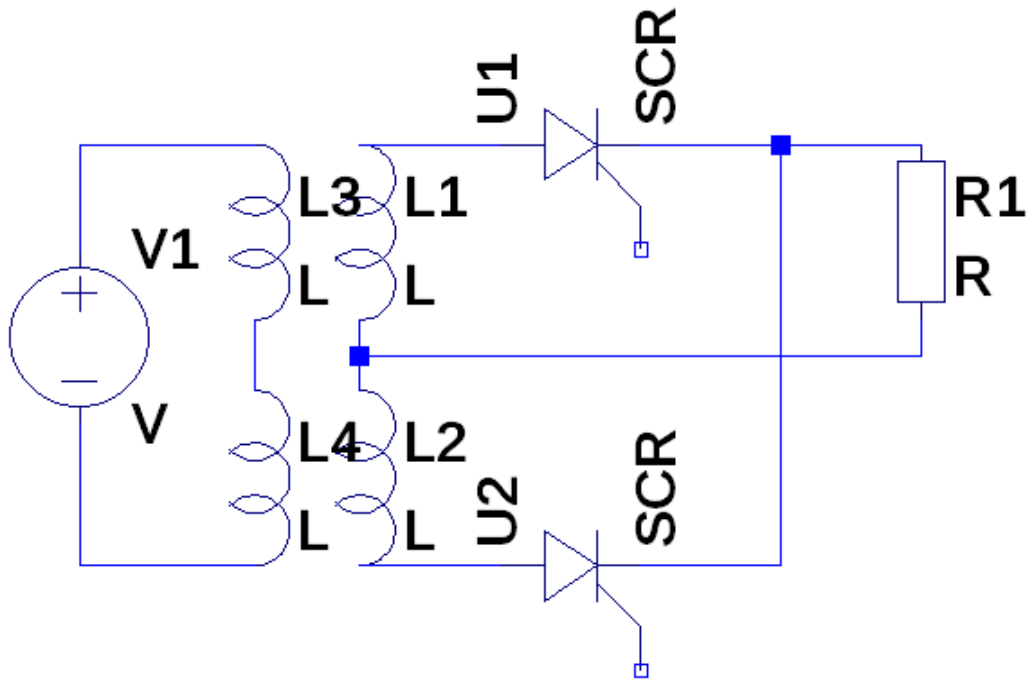


Lab 3: Controlled rectification

Part 1: Construction of rectifier power circuit.



Part 2: Commissioning of control circuit


Apply 6V to DC Voltage regulator input, check for 3.3V (approx) out.

Apply AC input (very carefully) and check voltage clamping by zener. Check output from 6N137 is a square wave.

Check voltage from potentiometer varies

Look for pulses coming from pins 9 and 10 of MSP430.

Connect Gates and Cathodes (K) to power circuit.

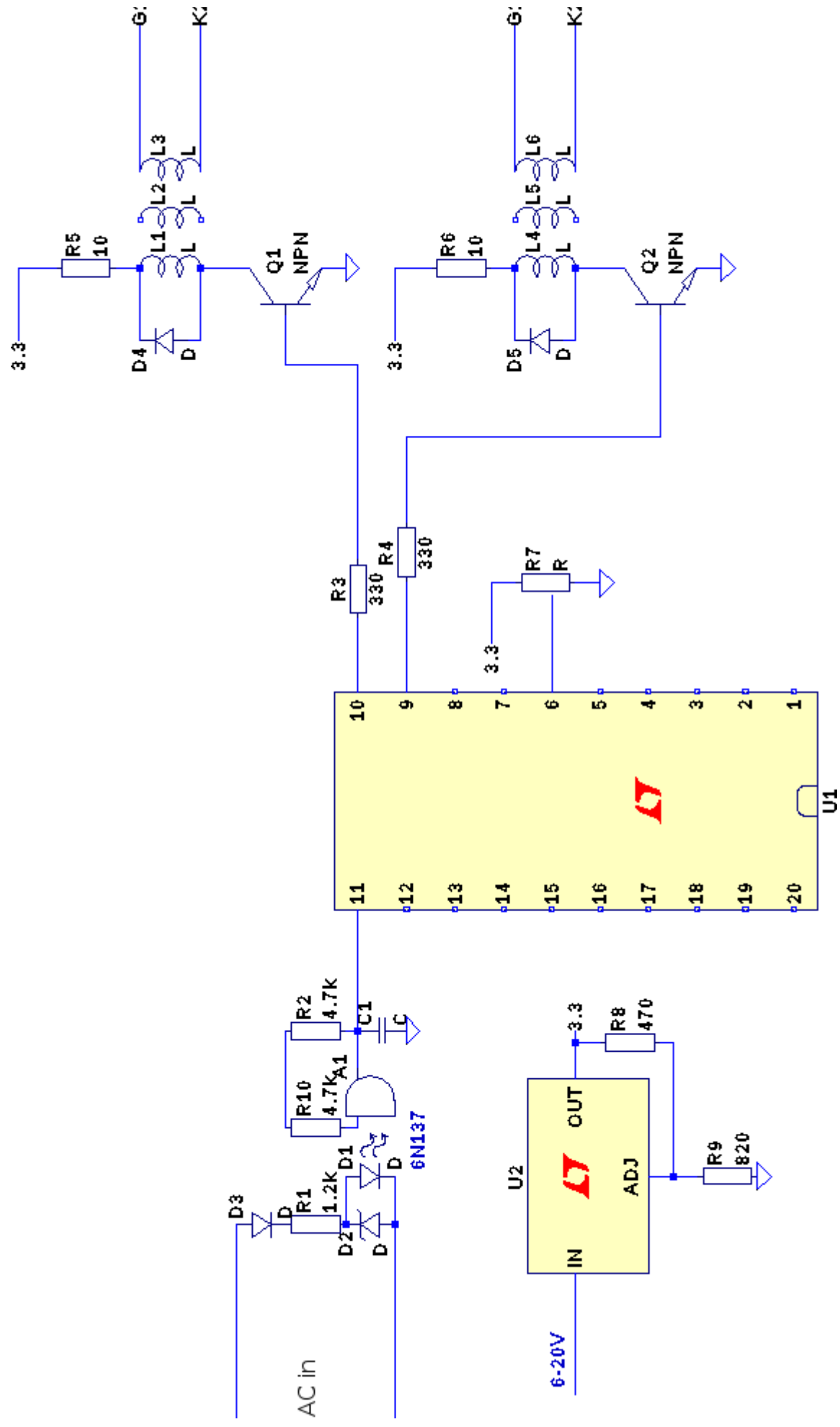

Part 3: Things to measure and record.

Average V_o vs firing angle.

Output waveform with resistive load

Output waveform with inductive load

Gate pulse waveform.

Questions:

What is meant by the terms **latching current** and **holding current**. – any evidence of either in circuit?

What would change for 240V operation?

Sketch a forced commutation circuit for a thyristor.

Appendix: Microcontroller code

```
void setup()
{
    // put your setup code here, to run once:
    pinMode(P2_1,OUTPUT);
    pinMode(P2_2,OUTPUT);
    pinMode(P2_3,INPUT);
    digitalWrite(P2_2,LOW);
    digitalWrite(P2_1,LOW);

}
void pulsePort(int Port)
{
    int i;

    {
        digitalWrite(Port,HIGH);
        __delay_cycles(10);
        digitalWrite(Port,LOW);
        __delay_cycles(10);
    }
}
void loop()
{
    // put your main code here, to run repeatedly:
    // Wait for rising edge on P1.1 (ZCD)
    while(digitalRead(P2_3)==0);
    delay(analogRead(P1_4)/100);

    pulsePort(P2_1);
    while(digitalRead(P2_3)!=0);
    delay(analogRead(P1_4)/100);

    pulsePort(P2_2);

}
```